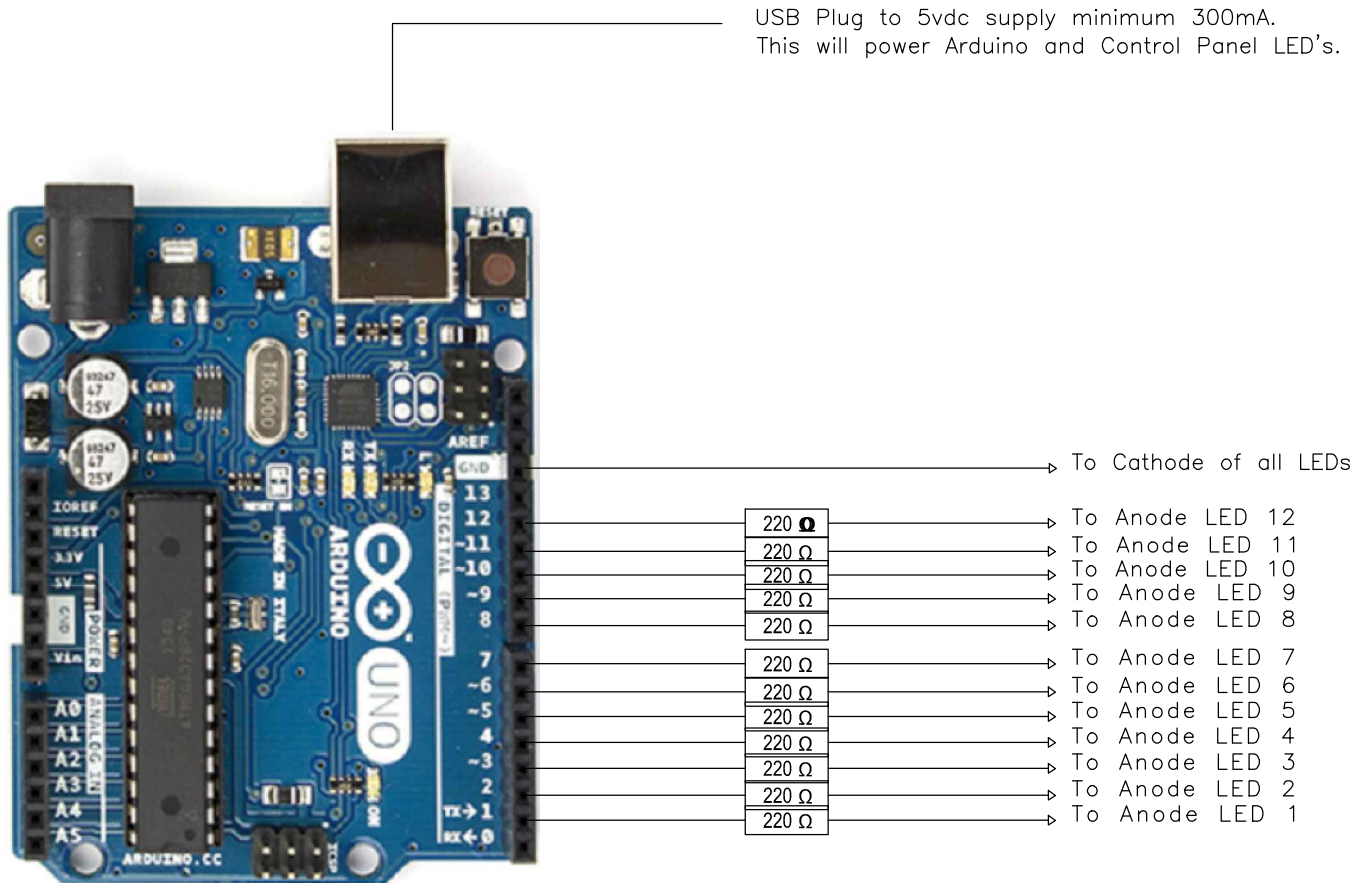


K9 Control Panel lighting using Arduino Uno

Control Panel LED arrangement .
Look from top



Components:

- 12x 220 Ω 0.25w Resistors
- 12x 5mm LEDs 400–1000 mcd 20mA (white LEDs if switches fitted with coloured lenses.)
- 1x Arduino Uno or clone.

Note:

Resistance calculated to limit current to 20mA
at 5Vdc for a typical 5mm LED.
Depending on LED selected resistance value can
be changed to alter brightness.

Keep in mind the maximum current output at
each pin on the Arduino is 40mA.

